



University of Bahrain

CE -- CIT -- UOB


TEST 1 (3 August 2015) ITCE263/EEG261: Electronics 1

Dr. Riyadh Al-Hakim

Q1. [30 marks]

Assume a **3.3 volt** Zener diode with $I_{z_{\min}} = 5 \text{ mA}$ and $P_{z_{\max}} = 1 \text{ W}$:

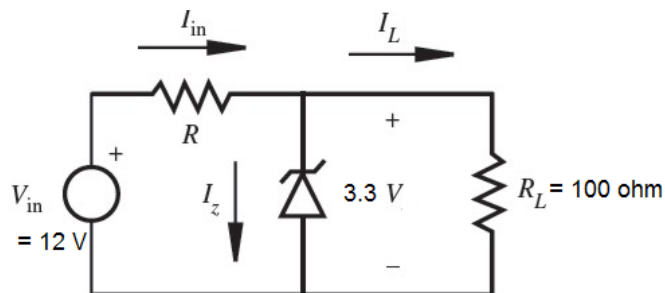1. If $R = 200 \text{ ohm}$, Find I_{in} , I_z and I_L
2. Find **minimum value of R** and **maximum value of R** that can be used in this simple voltage regulator (stabilizer) circuit



Q2. [30 marks]

A silicon diode has a **forward voltage = 0.6 volt** when the **current = 5 mA**. Find its static and dynamic resistances at **forward voltage = 0.7 volt**

Q3. [40 marks]

Assume $\beta = 100$

1. Find R for $V_{CE1} = 6 \text{ volt}$
2. Find I_c , I_E , I_B , V_{CE} and V_{CB} in both transistors
3. If you want to increase the 5 k resistance, what maximum value can you reach?

